

Designing Audio Power Amplifiers

Bob Cordell



New York Chicago San Francisco
Lisbon London Madrid Mexico City
Milan New Delhi San Juan
Seoul Singapore Sydney Toronto

Contents

Preface	xxix
Acknowledgments	xxxi

Part 1 Audio Power Amplifier Basics	1
1 Introduction	3
1.1 Organization of the Book	3
1.2 The Role of the Power Amplifier	4
1.3 Basic Performance Specifications	5
Rated Output Power	5
Frequency Response	5
Noise	6
Distortion	7
1.4 Additional Performance Specifications	7
Damping Factor	8
Dynamic Headroom	8
Slew Rate	9
Output Current	9
Minimum Load Impedance	10
1.5 Output Voltage and Current	10
1.6 Basic Amplifier Topology	11
1.7 Summary	14
References	14
2 Power Amplifier Basics	15
2.1 About Transistors	15
Current Gain	15
Base-Emitter Voltage	16
The Gummel Plot	17
Transconductance	18
Input Resistance	19
Early Effect	19
Junction Capacitance	20
Speed and f_T	21
The Hybrid Pi Model	23
The Ideal Transistor	23
Safe Operating Area	23
JFETs and MOSFETs	24
2.2 Circuit Building Blocks	25
Common-Emitter Stage	25

	Bandwidth of the Common-Emitter Stage and Miller Effect	27
	Differential Amplifier	28
	Emitter Follower	30
	Cascode	33
	Current Mirror	34
	Current Sources	36
	V_{be} Multiplier	40
2.3	Amplifier Design Analysis	41
	Basic Operation	42
	Input Stage	42
	The VAS	43
	Open-Loop Gain	44
	Miller Feedback Compensation	45
	The Output Stage	47
	Output Stage Bias Current	49
	Performance Limitations of the Simple Amplifier	50
	References	51
3	Power Amplifier Design Evolution	53
3.1	The Basic Power Amplifier	53
3.2	Adding Input Stage Degeneration	55
3.3	Adding a Darlington VAS	59
3.4	Input Stage Current Mirror Load	62
3.5	The Output Triple	64
3.6	Cascoded VAS	68
3.7	Paralleling Output Transistors	69
3.8	Higher-Power Amplifiers	72
3.9	Crossover Distortion	73
3.10	Performance Summary	75
3.11	Completing an Amplifier	75
	Input Network	75
	Feedback AC Decoupling Network	76
	Output Network	77
	Power Supply Decoupling	77
3.12	Summary	77
	References	77
4	Negative Feedback Compensation and Slew Rate	79
4.1	How Negative Feedback Works	79
4.2	Input-Referred Feedback Analysis	80
4.3	Feedback Compensation and Stability	81
	Poles and Zeros	81
	Phase and Gain Margin	82
	Gain and Phase Variation	84
4.4	Feedback Compensation Principles	84
	Dominant Pole Compensation	84
	Excess Phase	84

	Lag Compensation	85
	Miller Compensation	86
4.5	Evaluating Loop Gain	87
	Breaking the Loop	87
	Exposing Open-Loop Gain	89
	Simulation	89
4.6	Evaluating Stability	89
	Probing Internal Nodes in Simulation	90
	Checking Gain Margin	91
	Checking Phase Margin	91
	Recommendations	91
4.7	Compensation Loop Stability	92
4.8	Slew Rate	93
	Calculating the Required Miller Capacitance	93
	Slew Rate	94
	References	95
5	Amplifier Classes, Output Stages, and Efficiency	97
5.1	Class A, AB, and B Operation	97
5.2	The Complementary Emitter Follower Output Stage	98
	Output Stage Voltage Gain	99
	The Optimal Class AB Bias Condition	101
	Output Stage Bias Current	101
	gm Doubling	102
	The Small Class A Region of Many Amplifiers	103
5.3	Output Stage Efficiency	103
	Heat versus Sound Quality	104
	Estimating Power Dissipation	104
	Estimating the Input Power	104
	An Example	105
5.4	Complementary Feedback Pair Output Stages	105
	The Quasi-Complementary Output Stage	106
	The CFP Output Stage	106
	Biasing and Thermal Stability	107
	Optimum Class AB Bias Point and gm Doubling	107
	High-Frequency Stability	107
	Turn-Off Issues in CFP Output Stages	107
	Miller Effect in the CFP Output Stage	108
	CFP Triples	108
	CFP Degeneration	108
5.5	Stacked Output Stages	108
	Cascode Output Stage	110
	Soft Rail Regulation	110
5.6	Classes G and H	110
	Conflicting Terminology	110
	Class G Operation	111
	Class G Efficiency	113

Choice of Intermediate Rail Voltage	113
Headroom Considerations	113
Rail Commutation Diode Speed	114
The Transition to Cascode Operation	114
Safe Operating Area	114
5.7 Class D	115
References	115
6 Summary of Amplifier Design Considerations	117
6.1 Power and Loads	117
Worst-Case Loads	117
Peak Output Current	117
Slew Rate	118
6.2 Sizing the Power Supply	118
Average Power Supply Current	118
Sizing the Power Transformer	118
Sizing the Reservoir Capacitors	119
6.3 Sizing the Output Stage	119
Number of Output Pairs	119
6.4 Sizing the Heat Sink	120
A Simple Guideline	120
6.5 Protecting the Amplifier and Loudspeaker	121
Loudspeaker Protection	121
Short Circuit Protection	121
Safe Area Protection	121
6.6 Power and Ground Distribution	121
When Ground Is Not Ground	122
Ground Loops	122
Nonlinear Power Supply Currents	122
Current Flows Through the Shortest Path	122
6.7 Other Considerations	122
Output Stage Bias and Thermal Stability	122
Output Node Catch Diodes	123
Protection of Speaker Relay Contacts	123
Physical Design and Layout	123
The Feedback Path	123
References	123

Part 2 Advanced Power Amplifier Design Techniques 125

7 Input and VAS Circuits	127
7.1 Single-Ended IPS-VAS	127
Improved Single-Ended IPS-VAS	128
Shortcomings of the Single-Ended IPS-VAS	128
Opportunities for Further Improvement	130
Input Stage Stress	130

7.2	JFET Input Stages	131
	JFET Transistors	132
	JFET I_d versus V_{gs} Behavior	133
	JFET RFI Immunity	135
	Voltage Ratings	135
	JFET Input Pairs and Matching	136
7.3	Complementary IPS and Push-Pull VAS	136
	Complementary IPS with Current Mirrors	137
	Complementary IPS with JFETs	140
	Floating Complementary JFET-IPS	141
	Complementary IPS with Unipolar JFETs	142
7.4	Unipolar Input Stage and Push-Pull VAS	142
	Differential Pair VAS with Current Mirror	143
	IPS with Differential Current Mirror Load	144
7.5	Input Common Mode Distortion	146
7.6	Early Effect	147
7.7	Baker Clamps	148
7.8	Amplifier Noise	148
	Noise Power	148
	Noise Bandwidth	149
	Noise Voltage Density	149
	Relating Input Noise Density to Signal-to-Noise Ratio	149
	A-Weighted Noise Specifications	149
	VAS Noise	150
	Power Supply Noise	150
	Resistor Noise	151
	Shot Noise	151
	BJT Input Noise Current	152
	Noise of a Degenerated LTP	152
	JFET Noise	152
	Noise Simulation	153
	References	153
8	DC Servos	155
	8.1 Origins and Consequences of DC Offset	156
	Input Bias Current	156
	Conflicting Impedance Requirements	157
	Bypassed Equalizing Resistor	158
	DC-Coupled Feedback Network	158
	Complementary Input Stages	159
	DC Trim Pots	159
	JFET Input Stages	160
	8.2 DC Servo Basics	160
	DC Servo Architectures	161
	Setting the Low-Frequency Corner	161
	Amount of Offset to Be Corrected	162

	Servo Control Range	163
	Servo Clipping	163
	Servo Headroom	163
	The JFET Advantage	163
8.3	The Servo Is in the Signal Path	164
	Servo Op Amp Distortion and Noise	164
	Adding a Second Pole	165
8.4	DC Offset Detection and Protection	167
8.5	DC Servo Example	167
8.6	Eliminating the Input Coupling Capacitor	169
8.7	DC Servo Design Issues and Nuances	169
	Servo Start-Up Transients	169
	Low-Frequency Testing of Amplifiers	
	Employing Servos	169
	Simulation	169
9	Advanced Forms of Feedback Compensation	171
9.1	Understanding Stability Issues	172
	Dominant Pole Compensation	172
9.2	Miller Compensation	172
	Pole-Splitting	174
	Limitation on Slew Rate	174
	Distortion Reduction as a Free Side Benefit	175
	VAS Output Impedance	175
	The Feed-Forward Zero	176
	Inserting a Zero to Cancel or Mitigate a Pole	176
	Power Supply Rejection	177
	Buffered Miller Feedback Pick-Off Point	177
9.3	Two-Pole Compensation	177
	Conditional Stability	179
	Frequency Response Peaking and Overshoot	180
9.4	Miller Input Compensation	180
	Combining the Best of Input and Miller	
	Compensation	181
	Compensating the Compensation Loop	181
9.5	Transitional Miller Compensation	182
9.6	The Summing Node Pole	183
	References	183
10	Output Stage Design and Crossover Distortion	185
10.1	The Class AB Output Stage	185
	Class B or Class AB?	186
10.2	Static Crossover Distortion	186
	Crossover Distortion as a Function of Signal Level	188
10.3	Optimum Bias and Bias Stability	188
	Setting the Bias	189
	Bias Stability	189

	Dynamic Bias Stability	189
	The Bias Spreader	190
10.4	Output Stage Driver Circuits	190
	Darlington Output Stage	190
	The Triple	191
	The Diamond Driver	191
10.5	Output Transistor Matching Considerations	193
	Beta Matching	193
	Emitter and Base Resistance Matching	194
	Base Stopper Resistors	194
10.6	Dynamic Crossover Distortion	195
	Transistor Turn-Off Current Requirements	195
	An Example BJT Power Transistor	197
	Turning Off the Transistor under Conditions of	
	Beta Droop and f_T Droop	198
	The Role of Collector-Base Capacitance	198
	The Speedup Capacitor	199
	Current Slew Rate Requirements	200
10.7	The Output Emitter Resistors	200
	Power Dissipation	200
	Inductance	201
	Paralleled Emitter Resistors	201
10.8	Output Networks	201
	The Zobel Network	202
	Distributed Zobel Networks	203
	The Series L-R Network	203
	The Effect of the Coil on Sound Quality	203
	Variations on the Networks	204
	The Pi Output Network	204
	Eliminating the Output Coil	204
10.9	Output Stage Frequency Response and Stability	205
	Variation with Operating Point	205
	Base Stopper Resistors	206
	Load Capacitance	206
	Excess Phase	207
	Gain and Phase Margin	207
	Stabilizing the Triple	207
10.10	Sizing the Output Stage	209
	Power Dissipation	209
	Safe Operating Area	209
10.11	Delivering High Current	210
	Driving Low-Impedance Loads	210
	Loudspeaker Peak Current Requirements	210
	Beta Droop	210
	f_T Droop	211
	Safe Operating Area of the Driver	211

10.12	Driving Paralleled Output Stages	212
	Output Transistor Current Sharing	212
	Output Transistor Capacitances	212
10.13	Advanced Output Transistors	212
	References	213
11	MOSFET Power Amplifiers	215
11.1	MOSFET Types and Characteristics	216
	Lateral MOSFET Structure	217
	Vertical MOSFET Structure	218
11.2	MOSFET Advantages and Disadvantages	218
	Freedom from Second Breakdown and	
	Device Protection	218
	Fragile Gate Oxide	220
	The Body Diode	220
	Supply of High Current	220
	The Role of $R_{ds(on)}$	222
	Transconductance	222
	High Speed	223
	Transconductance Frequency Response	223
	MOSFET Disadvantages and Caveats	223
	MOSFETs versus Bipolar Transistors	224
11.3	Lateral versus Vertical Power MOSFETs	224
11.4	Parasitic Oscillations	225
	Gate Stopper Resistors	225
	Origin of Parasitic Oscillations	225
	MOSFET Internal Inductances	226
	MOSFET Output Capacitance	226
	Gate Zobel Networks	226
	Ferrite Beads	227
	Paralleled MOSFETs	227
	Spotting Parasitic Oscillations	227
11.5	Biasing Power MOSFETs	227
	$TC_{V_{gs}}$ Crossover Current	228
	Bias Spreaders for MOSFET Output Stages	228
	Dynamic Thermal Bias Stability	229
11.6	Crossover Distortion	231
	Transconductance Droop	231
	Absence of gm Doubling	232
	Use of Source Resistors	233
	Wingspread Simulations	233
	Memory Distortion	234
11.7	Driving Power MOSFETs	234
	Driving the Gate Capacitance	235
	Gate-Source Capacitance	235
	Gate-Drain Capacitance	235

Required Drive Current versus Slew Rate	236
Excess Phase at Signal Peaks	236
Driving Multiple Output Pairs	236
Maximum Drive Considerations	237
Gate Protection	237
Flying Catch Diodes	237
Natural Current Limiting	238
Short Circuit Protection	238
Folded Drivers	238
Boosted Driver Supplies	240
11.8 Paralleling and Matching MOSFETs	240
11.9 Simulating MOSFET Power Amplifiers	241
High-Frequency Simulations	243
11.10 A MOSFET Power Amplifier Design	243
References	243

12 Error Correction	245
12.1 Feed-Forward Error Correction	245
Reduced Effectiveness at High Frequencies	246
12.2 Hawksford Error Correction	246
A Specialized Form of Negative Feedback	247
Frequency Compensation	248
Effect on Output Impedance	248
12.3 Error Correction for MOSFET Output Stages	248
Simplified Error-Correction Circuit	249
Error-Correction Circuit Operating Voltage	250
Error-Correction Circuit Clipping	250
12.4 Stability and Compensation	250
Stability Considerations	251
Frequency Compensation Approach	251
Simulation of Effective Gain Crossover	
Frequency	252
Effect on the Global Feedback Loop	252
12.5 Performance and Design Issues	253
Trimming	253
High-Frequency Limitations	254
Nonlinearity in the Error Amplifier	254
Headroom and Clipping	255
Boosted Rails	255
Use with Low- V_{gs} MOSFETs	255
Error Correction for BJT Output Stages	256
12.6 Circuit Refinements and Nuances	257
Complementary Error Amplifier	257
CFP Error Amplifier	257
Cascode Drivers	258
References	259

13	Other Sources of Distortion	261
13.1	Distortion Mechanisms	261
13.2	Early Effect Distortion	262
13.3	Junction Capacitance Distortion	262
	MOSFET Gate Capacitance Nonlinearity	262
13.4	Grounding Distortion	263
13.5	Power Rail Distortion	263
	Output Stage Power Supply Rejection	264
13.6	Input Common Mode Distortion	264
	Testing for Common Mode Distortion	264
13.7	Resistor Distortion	264
13.8	Capacitor Distortion	266
13.9	Inductor and Magnetic Distortions	267
	Magnetic Core Distortion	267
	Distortion from Proximity to Ferrous Materials	268
	Ferrite Beads	268
13.10	Magnetic Induction Distortion	268
	Minimizing Magnetic Induction Distortion	268
13.11	Fuse, Relay, and Connector Distortion	268
	Fuse Distortion	269
	Relay Distortion	269
	Connector Distortion	272
13.12	Load-Induced Distortion	273
13.13	EMI-Induced Distortion	273
13.14	Thermally Induced Distortion (Memory Distortion)	273
	References	274

Part 3 Real-World Design Considerations 275

14	Output Stage Thermal Design and Stability	277
14.1	Power Dissipation versus Power and Load	277
14.2	Thermal Design Concepts and Thermal Models	279
	Temperature versus Log Time Plots	280
	Thermal Attenuation	280
	Lumped and Distributed Models	281
	Transient Thermal Impedance	281
	Thermal Simulation	282
	Measuring Heat Sink Thermal Resistance	284
14.3	Transistor Power Ratings	285
	Transistor Insulators	286
14.4	Sizing the Heat Sink	286
	Output Stage Power Dissipation	287
	Required Heat Sink Thermal Resistance	287
	Power Dissipation into Reactive Loads	287
	Transistor Junction Temperature	287
	The Thermal Breaker	288

	The Finger Test	288
	The Heat Sink Is Not Isothermal	288
	Sizing the Output Stage	288
14.5	The Bias Spreader and Temperature Compensation	290
	The V_{be} Multiplier	291
	V_{be} Multiplier Impedance	291
	V_{be} Multiplier Variations	293
	Darlington Bias Spreaders	294
	CFP Bias Spreaders	294
	Location of the Sensing Junction	295
	Isothermal Bias Spreader and Driver Circuit	296
	Thermal Attenuation Revisited	296
	Setting the Bias and the Temperature Compensation	297
	Biasing Lateral Power MOSFETs	297
	Biasing Vertical Power MOSFETs	298
14.6	Thermal Bias Stability	299
	Local Bias Stability	299
	Base Stopper Resistors and Thermal Bias Stability	302
	Measuring Thermal Bias Stability	302
	Bias Stability of MOSFETs versus BJTs	302
14.7	Thermal Lag Distortion	303
14.8	ThermalTrak™ Power Transistors	304
	Construction and Physical Characteristics	304
	Bias Spreaders Employing ThermalTrak™ Transistors	305
	Tracking Diode Temperature Characteristics	307
	Thermal Model	307
	Tracking Diode Response Time	309
	Thermal Attenuation	310
	Compensation of Predriver and Driver	310
	Bias as a Function of Time	310
	THD as a Function of Bias Setting	312
	ThermalTrak™ Transistors as Part of a Monitoring and Protection Scheme	313
	References	313
15	Safe Area and Short Circuit Protection	315
15.1	Power Transistor Safe Operating Area	315
	Secondary Breakdown Mechanism	316
	Temperature Derating of SOA	317
	Transient SOA	317
	Long-Term Reliability and Destruct Point	317
	Managing Risk	318
15.2	Output Stage Safe Operating Area	318
	Resistive Loads	318
	Reactive Loads	318

	Impedance and Conductance as a Function of Phase Angle	320
	Overlapped Elliptical Load Lines	322
15.3	Short Circuit Protection	323
	Rail Fuses	325
	Current Limiting	325
	A Simple Current Limiter	325
	Natural Current Limiting	326
	Shutdown Circuits	327
	Speaker Relays	328
	Load-Sensing Circuits	328
15.4	Safe-Area-Limiting Circuits	329
	Single-Slope $V-I$ Limiters	330
	Multi-Slope $V-I$ Limiters	331
	Drawbacks of $V-I$ Limiters	331
	Flyback Protection Diodes	333
	Avoiding the Use of $V-I$ Limiters	333
15.5	Testing Safe-Area-Limiting Circuits	333
	Simulation of Protection Circuits	334
15.6	Protection Circuits for MOSFETs	334
15.7	Protecting the Driver Transistors	334
15.8	Loudspeaker Protection Circuits	335
	Speaker Fuses	335
	The Speaker Relay and Its Control	335
	The TA7317 Loudspeaker Protection IC	336
	Protecting the Speaker Relay	338
	Closing the Feedback Loop Around a Protection Device ..	339
	Crowbar Circuits	340
	Avoiding Speaker Relays	340
	Protection Processors	341
	References	341
16	Power Supplies and Grounding	343
16.1	The Design of the Power Supply	343
	Alternative Supply Arrangements	343
	Boosted Supply Rails	344
	Power Supply Stiffness and Regulation	345
	Effective Power Supply Resistance	346
16.2	Sizing the Transformer	346
	VA Rating Rules of Thumb	347
	VA versus Weight	347
	Toroid versus Conventional	347
	Modifying Toroidal Transformers	348
16.3	Sizing the Rectifier	348
16.4	Sizing the Reservoir Capacitors	349
	Equivalent Series Resistance (ESR) and Inductance (ESL)	349

	Bypasses and Snubbers for Reservoir Capacitors	350
	Split Reservoir Capacitors	351
16.5	Rectifier Speed	351
	Soft Recovery and Fast Recovery	352
	Rectifier Noise and Snubbers	352
	Measuring Rectifier Performance	352
16.6	Regulation and Active Smoothing of the Supply	353
	Regulation of Input and VAS Power Supplies	354
16.7	SPICE Simulation of Power Supplies	354
16.8	Soft-Start Circuits	355
	Passive Soft-Start Circuits	355
	Active Soft-Start Circuits	356
16.9	Grounding Architectures	357
	Noisy and Quiet Grounds	357
	When Ground Is Not Ground	357
	Star Grounding	357
	Star-on-Star Grounding	358
	Ground Corruption	358
	Dual-Mono Designs	358
16.10	Radiated Magnetic Fields	359
	Antenna Loop Area	359
	Circuit Path Crossing Angle	359
16.11	Safety Circuits	359
	Safety Ground	359
	Breaking Safety Ground Loops	359
16.12	DC on the Mains	360
16.13	Switching Power Supplies	361
	References	362

17	Clipping Control and Civilized Amplifier Behavior	363
17.1	The Incidence of Clipping	363
	Clipping Experiments	364
17.2	Clipping and Sticking	364
17.3	Negative Feedback and Clipping	364
17.4	Baker Clamps	365
	Flying Baker Clamps and Flying	
	Catch Diodes	367
	Feedback Baker Clamps	367
17.5	Soft Clipping	368
	The Klever Klipper	368
17.6	Current Limiting	369
	Active Current Limiting	370
	Natural Current Limiting	370
17.7	Parasitic Oscillation Bursts	370
17.8	Optional Output Impedance	371
	References	371

18	Interfacing the Real World	373
18.1	The Amplifier-Loudspeaker Interface	373
	The Loudspeaker Is Not a Resistive Load	373
	Transmission Line Effects of Speaker Cables	375
18.2	EMI Ingress: Antennas Everywhere	376
	RFI and EMI	376
	EMI Ingress from the Amplifier Input	376
	Implications for Input Stage Design	378
	EMI Ingress from the Loudspeaker Cable	378
	Implications for Output Network Design	379
	Implications for Feedback Network Design	379
	EMI Ingress from the Mains	379
	EMI Distortion Mechanisms	379
18.3	Input Filtering	380
	Achieving a Linear Phase Response	380
18.4	Input Ground Loops	380
	Ground Break Resistor	380
	Balanced Inputs	380
	Interconnect Alternatives	381
18.5	Mains Filtering	381
	Line Filters	381
	Ferrites and Inductors	381
18.6	EMI Egress	381
18.7	EMI Susceptibility Testing	381
	Cell Phones and Electric Drills	381
	EMI Generators	382
	References	382

Part 4 Simulation and Measurement **383**

19	SPICE Simulation	385
19.1	LTspice	385
	Installation	385
	The Toolbars	386
	Control Panel	387
	Help	387
	The LTspice Users' Group	387
19.2	Schematic Capture	387
	Placing Components	388
	Picking and Placing Transistors	389
	Other Components and Subcircuit Libraries	389
	Parameterized Elements	389
	Completing the Schematic	389
19.3	DC, AC, and Transient Simulation	390
	The DC Operating Point	390
	The SPICE Error Log	391

	Convergence	391
	AC Analysis	392
	Transient Simulation	393
19.4	Distortion Analysis	394
	FFT Spectral Plots	394
	Optimizing FFT Simulations	395
	Total Harmonic Distortion	396
19.5	Noise Analysis	396
	Noise of Individual Contributors	397
	Weighted Noise Simulations	397
19.6	Controlled Voltage and Current Sources	397
19.7	Swept and Stepped Simulations	398
	DC Sweep	398
	DC Transfer	398
	Stepped Simulations	399
	Example: A Wingspread Simulation	399
19.8	Plotting Results	400
	Gummel Plot	401
	Beta versus I_c	402
	Transconductance versus I_c	402
19.9	Subcircuits	403
	Creating a Subcircuit	403
	The Symbol Editor	404
	Modifying an Existing Symbol	405
	Summary for Creating the LPF1 Symbol	405
	Using the Subcircuit in a Schematic	405
	Installing Subcircuit Models in a Library	405
19.10	SPICE Models	406
	Bipolar Junction Transistors	406
	Junction Field Effect Transistors	406
	Power MOSFETs	407
	Include Statements	408
	Libraries	408
19.11	Simulating a Power Amplifier	408
	DC Analysis	409
	Frequency Response	410
	1-kHz Transient Analysis	410
	20-kHz Transient Analysis	410
	Square-Wave Response	411
	1-kHz Total Harmonic Distortion	411
	20-kHz THD	412
	CCIF Intermodulation Distortion	413
	Signal-to-Noise Ratio	414
	Damping Factor and Output Impedance	415
	Stability	415
	Inferring Loop Gain	415

	Measuring Loop Gain	416
	Output Stage Power Dissipation	416
	Output Current Limiting	416
	Safe Operating Area	416
	References	417
20	SPICE Models and Libraries	419
20.1	Verifying SPICE Models	420
	The Hybrid Pi Model	420
20.2	Tweaking SPICE Models	421
	A Typical SPICE Model File	421
	Base-Emitter Voltage	422
	Current Gain	423
	Speed	423
	Base-Emitter Capacitance	424
	Base-Collector Capacitance	424
20.3	Creating a SPICE Model	424
	Gathering Data Sheet Information	425
	Measuring Device Data	425
	Saturation Current and Nominal V_{be}	425
	Early Voltage	427
	Nominal Beta	429
	Beta Droop at High and Low Current	429
	Establish RB	433
	Establish RB at High Base Current	434
	Establish Nominal Transit Time and f_T	435
	Establish f_T Droop at High Current	435
	Establish f_T Droop at Low Voltage and High Current	437
	Establish f_T Droop at Low Current	437
	Determine Base-Collector Capacitance	439
	Check the Model	439
	BJT Model Example	439
20.4	JFET Models	440
	DC Behavior of JFETs	440
	The JFET SPICE Model	441
	Creating and Tweaking the JFET Model	441
20.5	Vertical Power MOSFET Models	442
	Establishing the DC Parameters	442
	Gate-Source Capacitance	443
	Gate-Drain Capacitance	444
	C_{gd} Test Circuit	444
	The Subcircuit Model	445
	Subthreshold Conduction	446
	Applicability	447
	Power Amplifier Design Concerns	447

20.6	LTspice™ VDMOS Models	447
	Establishing the Model Parameters	448
	Applicability	449
20.7	The EKV Model	450
	Subthreshold MOSFET Measurements	452
	Model Creation Procedure	453
	Applicability	454
20.8	Hybrid VDMOS-EKV Model	454
20.9	Lateral Power MOSFETs	455
20.10	Installing Models	456
	References	456
21	Audio Instrumentation	459
21.1	Basic Audio Test Instruments	459
	Audio Oscillator	459
	AC Voltmeter	460
	Oscilloscope	460
21.2	Dummy Loads	460
	Choose Load Resistors Wisely	460
	Inductive versus Noninductive	460
	Power Dissipation and Cooling	461
	Connecting to the Dummy Load	461
21.3	Simulated Loudspeaker Loads	461
	Protection Circuit Testing	462
21.4	THD Analyzer	462
	Interpreting Results	463
	Spectral Analysis	463
	Obtaining a THD Analyzer	464
21.5	PC-Based Instruments	464
	Sound Card Software	464
	Sound Cards	465
	PC-Based Oscilloscopes	465
21.6	Purpose-Built Test Gear	465
	Sound Card Interface Boxes	465
	The Distortion Magnifier	466
	Balanced Interfaces	467
	IM Test Signal Combiner	468
	Synchronous Tone Burst Generator	468
	Signal-to-Noise Measurement Preamp with A Weighting	469
	Powering Purpose-Built Test Equipment	469
	References	470
22	Distortion and Its Measurement	471
22.1	Nonlinearity and Its Consequences	471
	The Order of a Nonlinearity	472

22.2	Total Harmonic Distortion	472
	Interpretation of THD	472
	Advantages of THD	473
	Limitations of THD	474
22.3	SMPTE IM	474
22.4	CCIF IM	475
22.5	TIM and SID	476
	Slew Rate Limiting and Input Stage Stress	476
	The DIM Test	477
	THD-20 Will Always Accompany TIM	477
22.6	PIM	478
	Differential Gain and Phase	478
	Measuring PIM	479
	Negative Feedback and PIM	479
	Input Stage Stress	480
	PIM in Amplifiers Without Negative Feedback	480
22.7	IIM	480
	Loudspeaker emf and Peak Current Requirements	481
	High-Current Amplifier Design	482
	Measuring IIM	482
	Open-Loop Output Impedance	483
22.8	Multitone Intermodulation Distortion	484
22.9	Highly Sensitive Distortion Measurement	484
22.10	Input-Referred Distortion Analysis	485
	Input Referral Breaks the Feedback Loop	485
	Input Referral Demonstrates Why High Forward-Path Gain Reduces Distortion	485
	References	486
23	Other Amplifier Tests	489
23.1	Measuring Damping Factor	489
23.2	Sniffing Parasitic Oscillations	490
23.3	EMI Ingress Susceptibility	491
23.4	Burst Power and Peak Current	492
23.5	PSRR Tests	493
23.6	Low-Frequency Tests	493
	Beat Frequency Tests	493
23.7	Back-Feeding Tests	494
	Back-Fed Beat Frequency Test	494
	THD-20 in the Presence of Low-Frequency Back-Feed	494
	Current-Induced Distortion Tests	495
	References	495

Part 5	Topics in Amplifier Design	497
24	The Negative Feedback Controversy	499
24.1	How Negative Feedback Got Its Bad Rap	499
	Amplifier Limitations of the 1970s	499
	Guilt by Association	499
	TIM, PIM, and IIM	500
24.2	Negative Feedback and Open-Loop Bandwidth	500
	The Input Stage Error Signal	500
24.3	Spectral Growth Distortion	502
	Baxandall's Findings	502
	Real-World Amplifiers	503
	Degeneration and SGD	503
	SGD and Crossover Distortion	504
24.4	Global versus Local Feedback	505
24.5	Timeliness of Correction	505
24.6	EMI from the Speaker Cable	505
24.7	Stability and Burst Oscillations	505
24.8	Clipping Behavior	506
	References	506
25	Amplifiers Without Negative Feedback	509
25.1	Design Trade-Offs and Challenges	509
	Input Stage Dynamic Range and Distortion	510
	JFET Input Buffers	512
	Cascodeing the Input Stage	512
	Gain Allocation	512
	Controlling VAS Gain	513
	VAS Noise	514
	Amplifiers with Local Negative Feedback	515
	Output Stage Distortion	515
	MOSFET Output Stages	516
	Damping Factor	517
	Power Supply Rejection and Power Supply Design	518
	DC Offset	518
	Balanced Inputs	519
25.2	Additional Design Techniques	519
	A Complementary IPS-VAS	519
	The Cascomp Input Stage	520
25.3	An Example Design with No Feedback	522
25.4	A Feedback Amplifier with Wide Open-Loop	
	Bandwidth	524
	Achieving Wide Open-Loop Bandwidth	524
	A 200-W MOSFET Design	524
	References	526

26	Balanced and Bridged Amplifiers	527
26.1	Balanced Input Amplifiers	527
	Gain and Input Impedance Considerations	527
	Single and Triple Op-Amp Solutions	528
	Configuring the Power Amplifier as a Differential Amplifier	529
	The Differential Complementary Feedback Quad (DCFQ)	530
26.2	Bridged Amplifiers	531
	Sound Quality	532
	Power Supply Advantages	532
26.3	Balanced Amplifiers	533
	True Balanced Amplifiers	533
	Differential-Mode Feedback	533
	Differential-Mode DC Servo	534
	Common-Mode DC Servo	534
27	Integrated Circuit Power Amplifiers and Drivers	537
27.1	IC Power Amplifiers	537
27.2	The Gain Clones	538
	A Basic Gain Clone Design	538
	A Gain Clone Using the Inverting Mode	538
	Avoiding Electrolytic Capacitors While Controlling Offset	539
27.3	The Super Gain Clone	539
	Input Circuits	539
	Power Amplifier	541
	Output Network	541
	DC Servo	541
	Performance	541
27.4	Integrated Circuit Drivers	542
	The LME49810	542
	The LME49830	544
27.5	An Integrated Circuit Bias Controller	544
	Compensation of the Amplifier	547
	Compensation of the LT1166	548
	A Non-Switching Amplifier	548
	A MOSFET Power Amplifier Using the LT1166 and LME49830	548
27.6	Summary	550
	References	550

Part 6 Class D Amplifiers **551**

28	Class D Audio Amplifiers	553
28.1	How Class D Amplifiers Work	554
	Analog Class D and Digital Class D	555
	Synchronous and Asynchronous Class D	555

28.2	Buck Converters	555
	Synchronous Buck Converter	557
	Gate Drive Requirements and Power Dissipation	558
	Gate Charge	558
	MOSFET Figure of Merit	560
	Conduction Loss	560
	Switching Loss	561
	Reverse Recovery Loss	561
28.3	Class D Output Stages	562
	Single-Ended and H-Bridge Output Stages	562
	N-Channel Output Stages	562
	Gate Drive Control	563
	Dead Time Control	563
	Adaptive Dead Time Control	564
28.4	Summary	564
	References	564
29	Class D Design Issues	565
29.1	The Output Filter and EMI	565
	The Zobel Network	567
	Differing Loudspeaker Impedance	567
	Linear Phase Approximation	567
	Reducing Output Filter Size	567
	Input Filter and Aliasing	568
	Other EMI Issues	568
	Output Filter Distortion	568
29.2	Sources of Distortion	569
	Triangle Reference Linearity and Bandwidth	569
	Pulse Width Quantization	569
	Dead Time	569
	PWM Crossover Distortion	571
	The PWM Central Region	572
	Extending the PWM Central Region	573
	Asymmetrical Rise/Fall Times	573
	Body Diode Conduction Time	573
	Sliver Pulses	573
29.3	Bus Pumping	574
29.4	Power Supply Rejection	575
	Loop Gain Modulation	576
	Power Supply Feedback to the Triangle Generator	576
29.5	Power Supplies for Class D Amplifiers	576
	Linear Power Supplies	576
	Switching Power Supplies	577
29.6	Negative Feedback	577
	Closing the Loop Before the Output Filter	578
	Closing the Loop Around the Output Filter	579

29.7	Damping Factor and Load Invariance	580
29.8	Summary	581
	References	581
30	Alternative Class D Modulators	583
30.1	Self-Oscillating Loops	583
	Self-Oscillation with Pre-filter Feedback	584
	Self-Oscillation with the Output Filter	585
	Self-Oscillation Using a One-Shot	585
	Synchronized Self-Oscillating Loops	586
30.2	Sigma-Delta Modulators	587
	Oversampling	588
	High-Speed Class D Sigma-Delta Amplifiers	589
	High Sigma-Delta Modulator Clock Frequencies	590
	Adaptive Transition Density Limiting	590
	Noise Shaping	590
	Second-Order Sigma-Delta Modulators	591
	Higher-Order Sigma-Delta Modulators	592
	EMI of Sigma-Delta Class D Amplifiers	592
	The Output Filter	592
	Post-Filter Feedback	592
30.3	Digital Modulators	593
	Digital PWM Modulators	593
	Digital Sigma-Delta Modulators	593
	Feedback and PSRR	593
	References	594
31	Class D Measurement, Performance, and Efficiency	595
31.1	Hybrid Class D	595
31.2	Measuring Class D Amplifiers	597
	The AES17 Filter	597
	Total Harmonic Distortion	597
	SMPTE IM	598
	CCIF Tests	598
	Aliasing	598
	PSRR	598
	Conductive Emissions	599
31.3	Achievable Performance	599
	Efficiency	599
	Distortion	599
	References	600
	Index	601